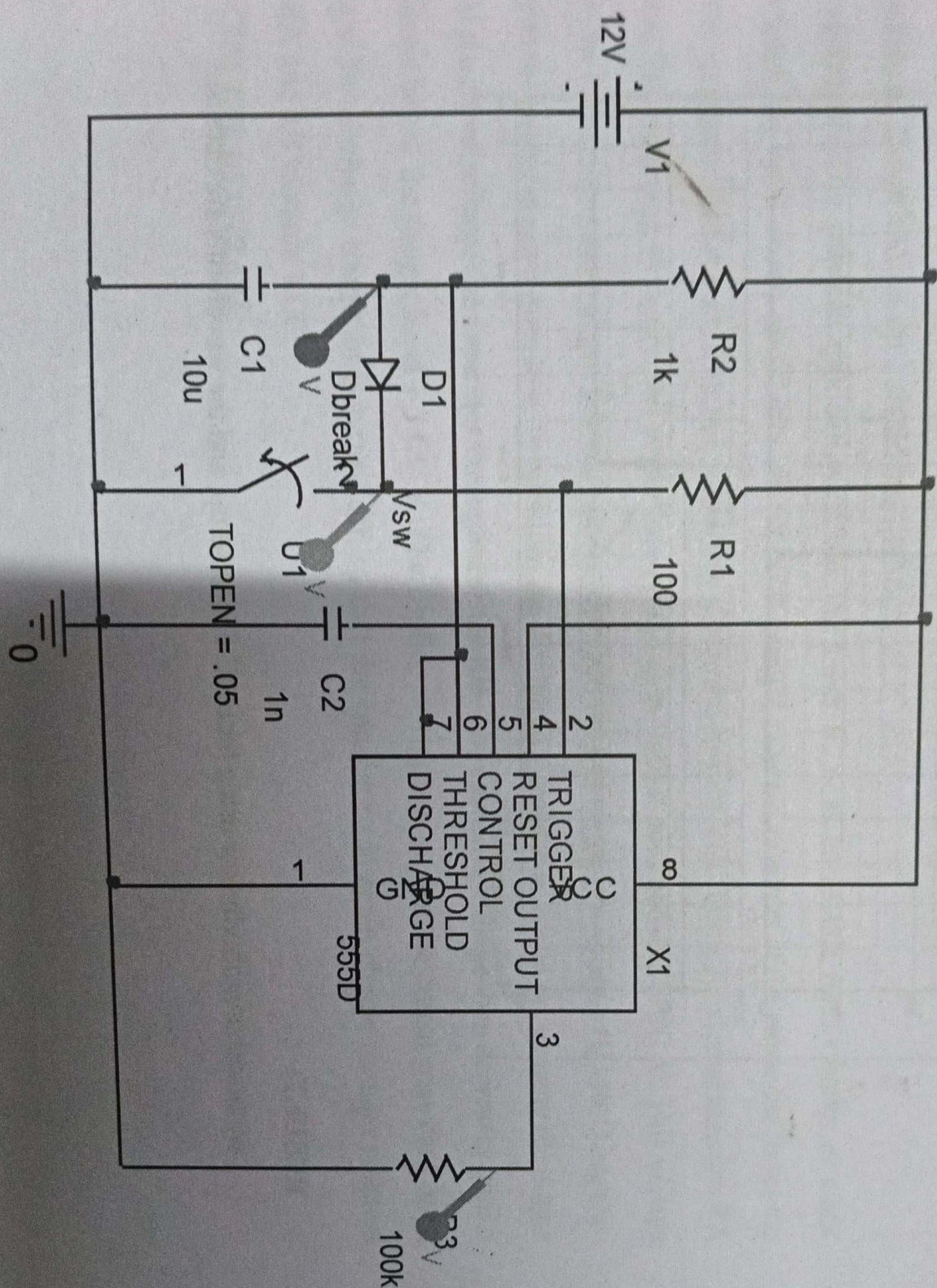


monistable multivibrator using 555


CIRCUIT DIAGRAM:



astable multivibrator using 555 timer

MVJCE

DEPT. OF ACT

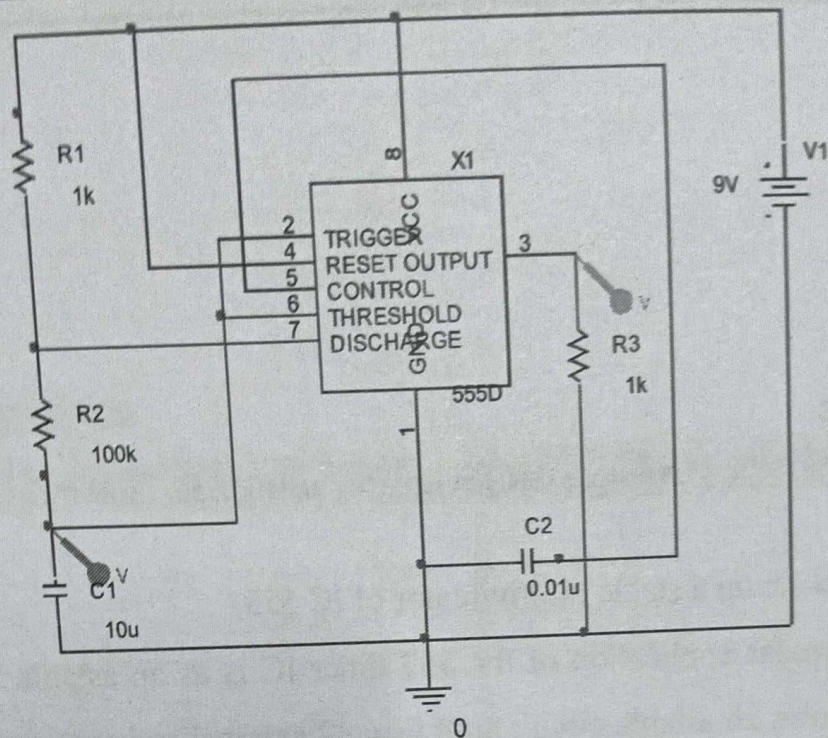


SIMULATION PROFILE:

Time domain analysis

Run to time=6s


Start saving data after=1s

EXPECTED WAVEFORM

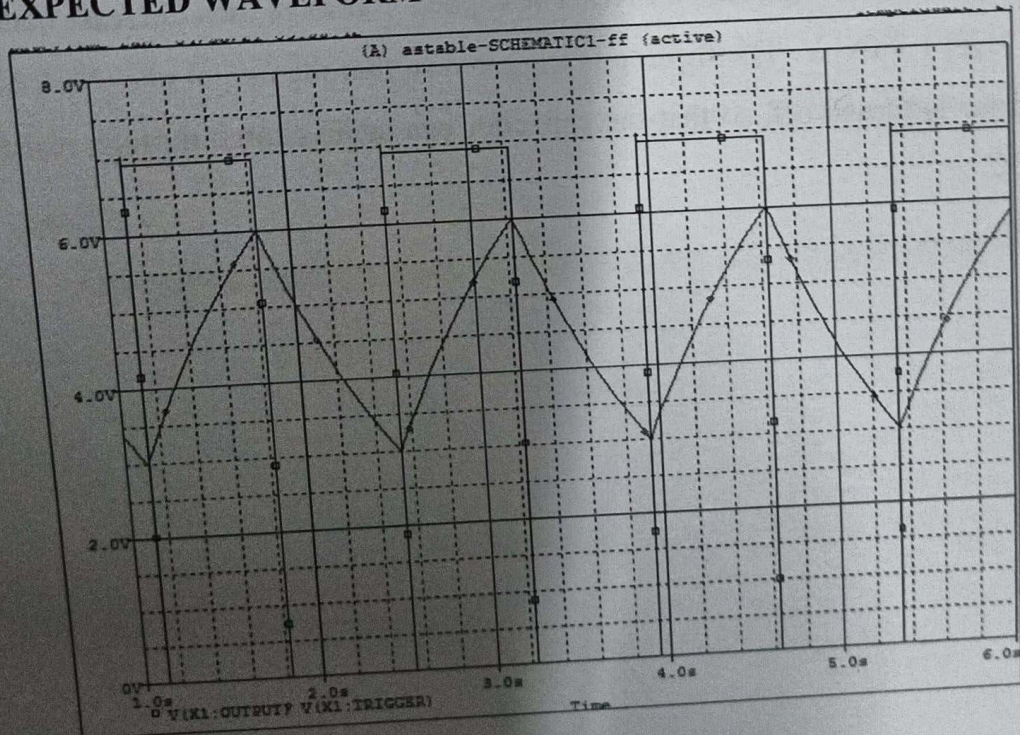

RESULT:

rc phase shift

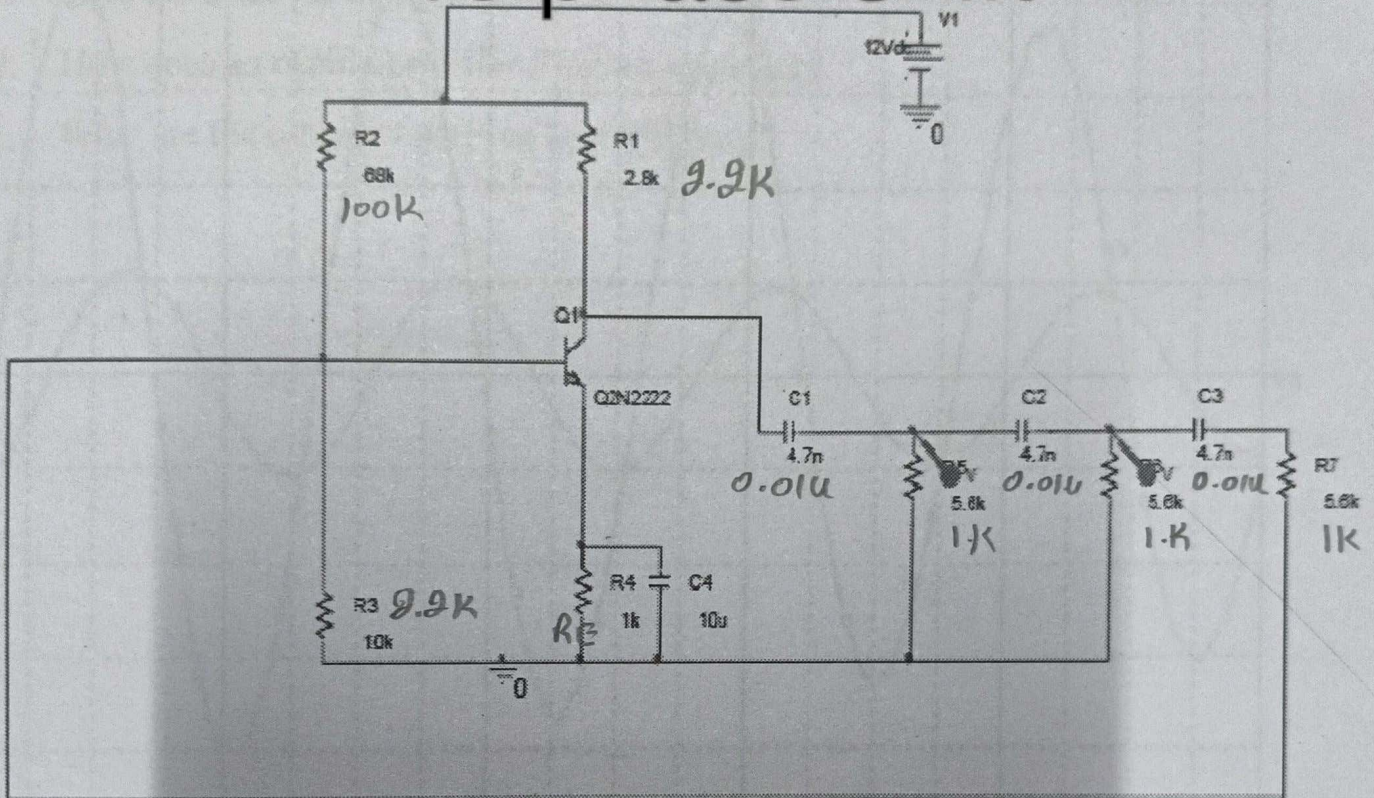

Simulation Profile:

Time domain analysis

Run to time=1ms

Start saving data after=0ms

Maximum step size = 0


Output Waveform:

Aim: Test a comparator circuit and design a Schmitt trigger for the given UTP and LTP values and obtain the hysteresis

Theory:

A Schmitt trigger or a squaring circuit converts an irregular shaped waveform to a square wave or pulse. This also gives an output waveform virtually discontinues at the comparison voltage and it also exhibits a phenomenon called hysteresis.

Circuit Diagram:

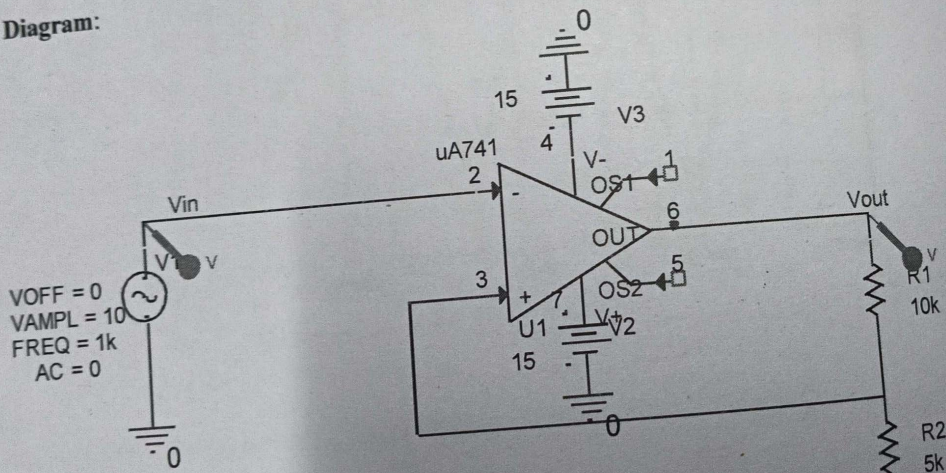


inverting schmitt trigger

Steps to ob

1. Util
2. Wh
- Set
3. W
- for
4. O
5. S
- 3
6. I
- 7.

Circuit Diagram:

Band Pass Filter

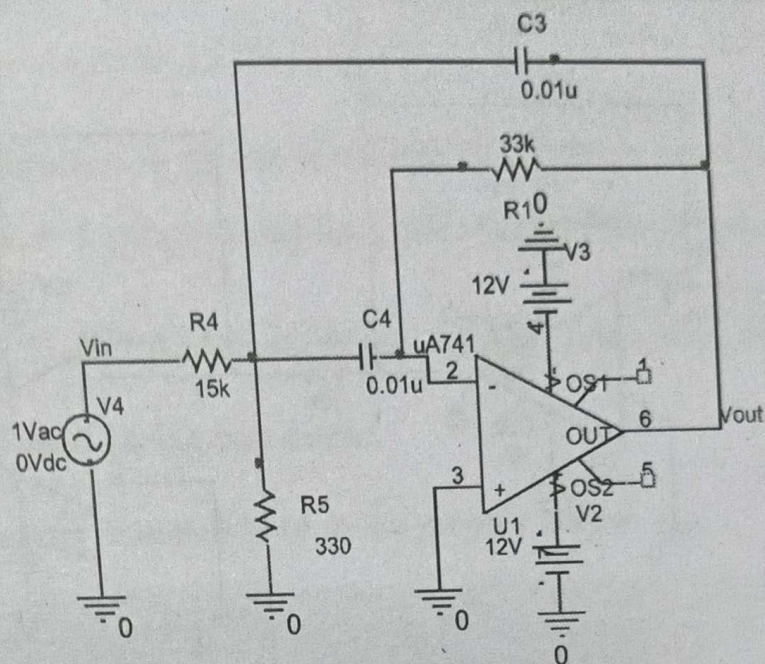

SIMULATION PROFILE

AC Sweep Time


Logarithmic-Decade

Start Frequency = 1


End Frequency = 1G

Points/Decade = 10

EXPECTED GRAPH

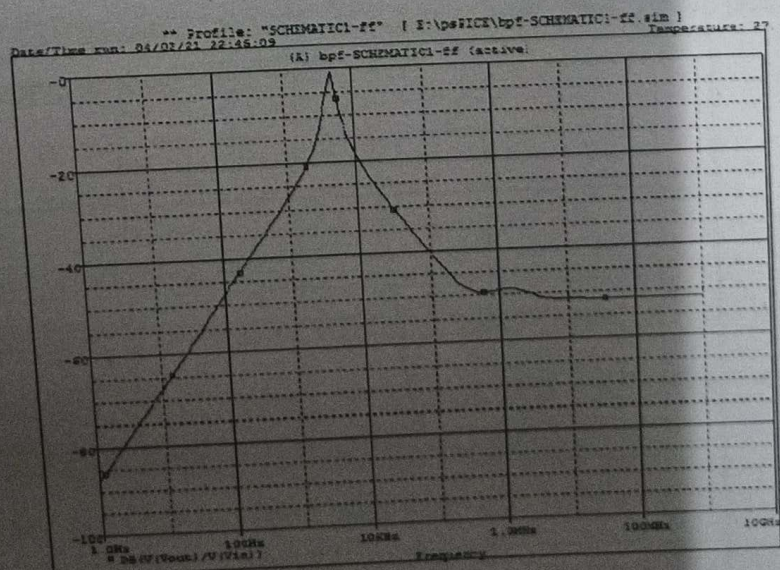

Band Reject Filter

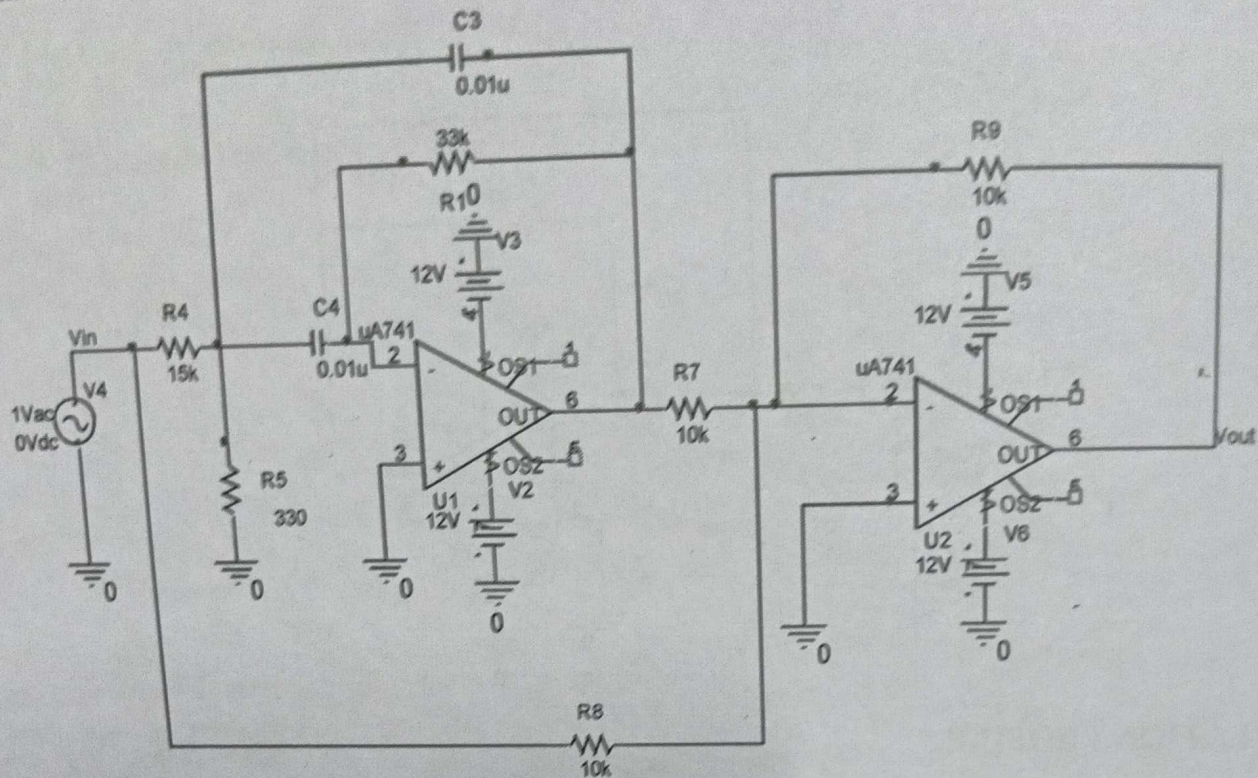

SIMULATION PROFILE

AC Sweep Time


Logarithmic-Decade

Start Frequency = 1

End Frequency = 100k

Points/Decade = 10

EXPECTED GRAPH

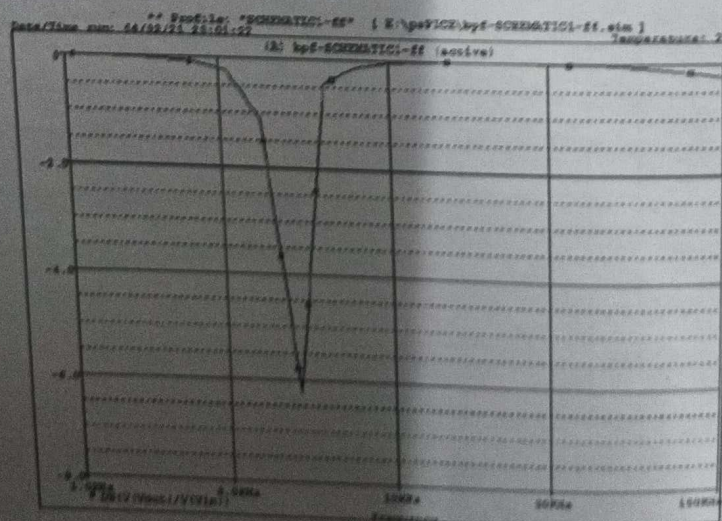


PRECISION RECTIFIERS

Aim: To simulate the performance of half wave and full-wave precision rectifier using op-amp

Theory:

The major limitation of ordinary diode is that it cannot rectify voltages below $V_r(0.6v)$, the cut-in voltage of the diode. A circuit which is capable of rectifying input signals of the order of mv is called as precision rectifier.

Circuit Diagram:

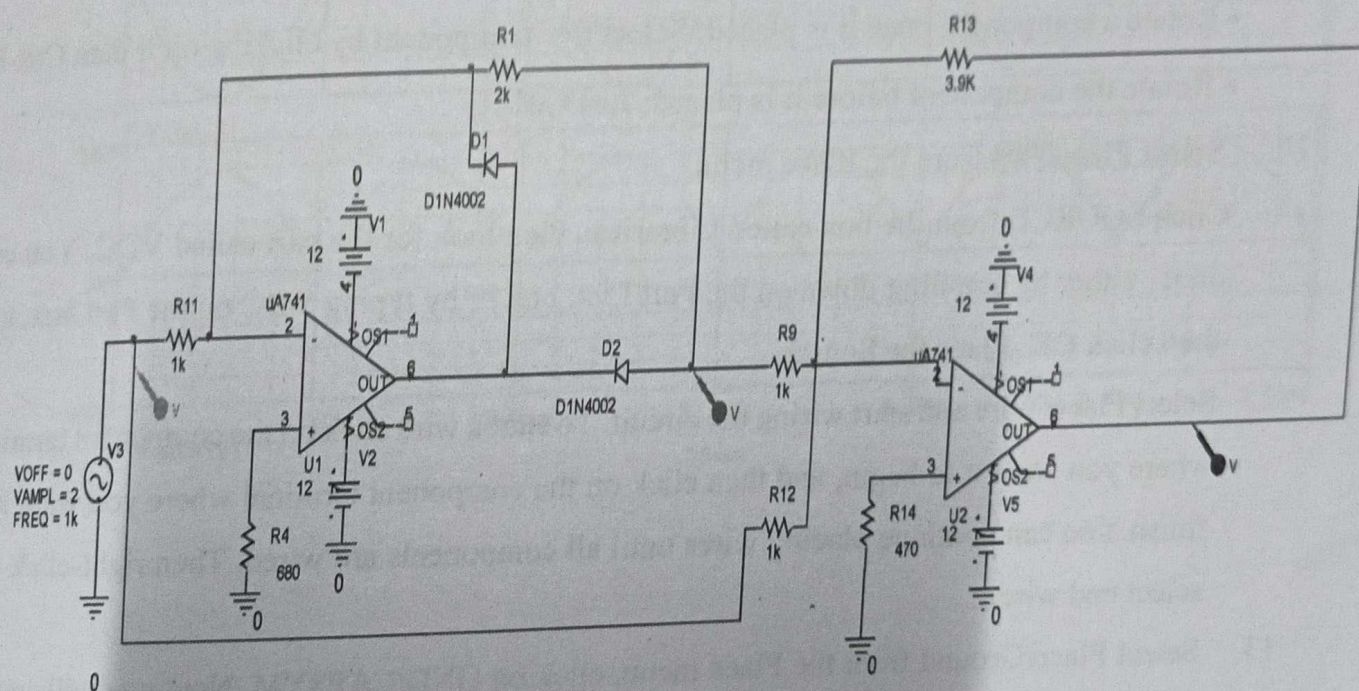

Procedure:

Steps for Simulation of circuit using PSpice

1. Run the CAPTURE program.
2. Select File/New/Project from the File menu.
3. On the New Project window select Analog or Mixed A/D, and give a name to your project then click OK.
4. The Create PSpice Project window will pop up, select Create a blank project, and then click OK.